

Hardware Modeling

VHDL - Architectures

*Vienna University of Technology
Department of Computer Engineering
ECS Group*

Contents



- ▶ Structural Modeling
 - Instantiation of Components
- ▶ Behavioral Modeling
 - Processes
 - Concurrent Signal Assignments
- ▶ Mixed Modeling

Ways of Modeling a Circuit



```
architecture xyz of abc is  
begin
```



```
end architecture xyz;
```





Ways of Modeling a Circuit

```
architecture xyz of abc is  
begin
```

Behavioral

```
if A = '1' then    D <= NOT E  
    B <= B+1  
else  
    B <= B  
end if  
  
F <= D OR B  
  
C <= F AND A
```


Structural

  

```
end architecture xyz;
```

Structural Modeling

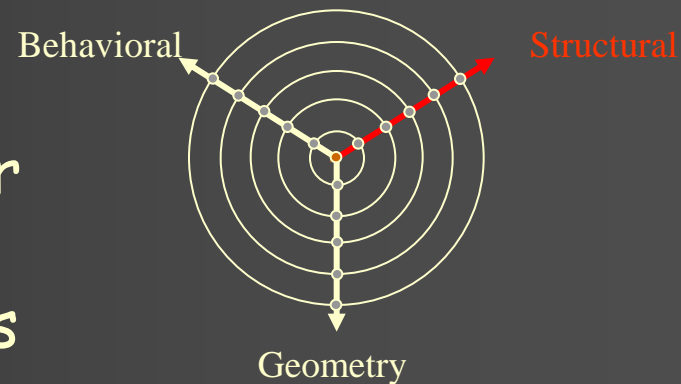- ▶ Instantiation of components
- ▶ Either **graphically** (Schematic) or **textually** (VHDL, Verilog, ...)
- ▶ Connections between components created by **wires** (graphically) or **port maps**



Attention: Possibility of getting dependent on a certain technology or vendor specific libraries!



Instantiation of Components



▶ Component Declaration

Describes the component's **interface**
(best to be done within a package, but also possible in the declaration part of an architecture or block)

▶ Component Instantiation

Assignment of signals to the component interface

▶ Component Configuration

Functionality selection for each component



Declaration of a Component

Architecture

```
architecture struct of abc is
  component one
    generic
      (
        DEPTH : integer := 8
      );
    port
      (
        a, b : in bit;
        c    : out bit
      );
    end component one;
  begin
    .....
  end architecture struct;
```

Package

```
package my_pkg is
  component one
    generic
      (
        DEPTH : integer := 8
      );
    port
      (
        a, b : in bit;
        c    : out bit
      );
    end component one;
  .....
end package my_pkg;
```

Instantiation of a Component (1)



- ▶ Three important terms:
 - **formals** Ports and generics of the instantiated entity
 - **locals** Ports and generics of the component declaration
 - **actuals** Signals (parameters) within the architecture

- ▶ When instantiated: *Locals* get connected to *actuals* (\Rightarrow port map, generic map)


Instantiation of a Component (2)

```
use work.my_pkg.all;

architecture struct of xyz is
  signal s1, s2, s3, s4: bit;
begin
  --named association
  one_inst1 : one
    generic map(DEPTH => 10)
    port map(a => s1, b => s2,
             c => s3);
  --positional association
  one_inst2 : one
    generic map(10)
    port map(s3, s2, s4);
end architecture struct;
```

2 instances
of one

Default value is
replaced by 10

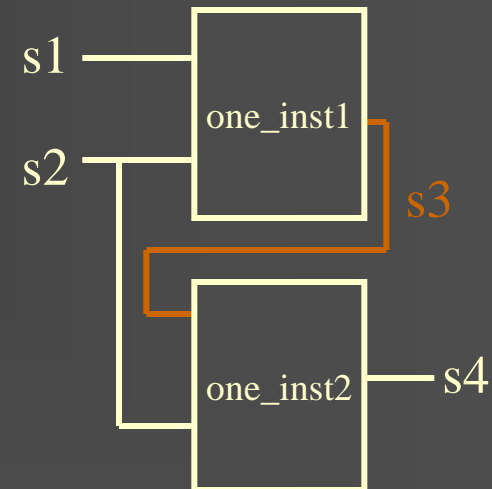

Conditional Instantiation

▶ if-generate statement

```
.....  
  
if boolean expression generate  
  one_inst1 : one  
    generic map(DEPTH => 10)  
    port map(a => s1, b => s2,  
             c => s3);  
end generate;  
  
.....
```

Parallel Instantiation (1)

▶ for-generate statement

```
.....  
  
-- s1, s2 and s3 are declared as:  
-- bit_vector(0 to 4)  
for i in 0 to 4 generate  
    one_inst1 : one  
        generic map(DEPTH => 10)  
        port map(a => s1(i), b => s2(i),  
                c => s3(i));  
end generate;  
  
.....
```

Parallel Instantiation (2)

```
.....  
-- s1, s2 and s3 are declared as:  
-- bit_vector(0 to 4)  
for i in 0 to 4 generate  
  signal tmp : bit;  
begin  
  one_inst1 : one  
    generic map(DEPTH => 10)  
    port map(a => s1(i), b => s2(i),  
            c => tmp);  
  
  one_inst2 : one  
    generic map(DEPTH => 10)  
    port map(a => tmp, b => s2(i),  
            c => s3(i));  
end generate;
```

```
.....
```

Component Configuration

- ▶ **Implicit configuration**, if only one architecture for the component exists
- ▶ **Explicit configuration** done in the design unit's configuration:

```
configuration xyz_cfg of xyz is
  for struct
    for one_inst1 : one use work.one(struct);
    for one_inst2 : one use work.one(beh);
  end for;
end configuration xyz_cfg;
```

- ▶ **or directly at instantiation:**

```
one_inst1 : entity work.one(struct)
  generic map ...
```

Component Configuration

- ▶ **Implicit configuration**, if only one architecture for the component exists
- ▶ **Explicit configuration** done in the design unit's configuration:

```
configuration xyz_cfg of xyz is
  for struct
    for one_inst1 : one use work.one(struct);
    for one_inst2 : one use work.one(beh);
  end for;
end configuration xyz_cfg;
```

- ~~▶ or directly at instantiation:~~

```
one_inst1 : entity work.one(struct)
  generic map ...
```

Structural Modeling - Summary



- ▶ Three steps
 - Component declaration
 - Component instantiation
 - Component configuration
- ▶ Connections between components are modeled using port mapping
- ▶ Parameters are set through generic mapping
- ▶ Possibility for conditional and parallel instantiation




Contents



- ▶ Structural Modeling
 - Instantiation of Components
- ▶ Behavioral Modeling
 - Processes
 - Concurrent Signal Assignments
- ▶ Mixed Modeling

Behavioral Modeling

 - ▶ How to model the behavior of hardware?
 - Hardware may work parallel or sequential
 - Input changes may trigger output changes at arbitrary times
 - How to model time and delay?



Behavioral Architecture



```
architecture beh of abc is  
begin
```



Time & delay

if ... then

for ... loop


Spikes and races

```
end architecture beh;
```

case ... when



Processes (1)

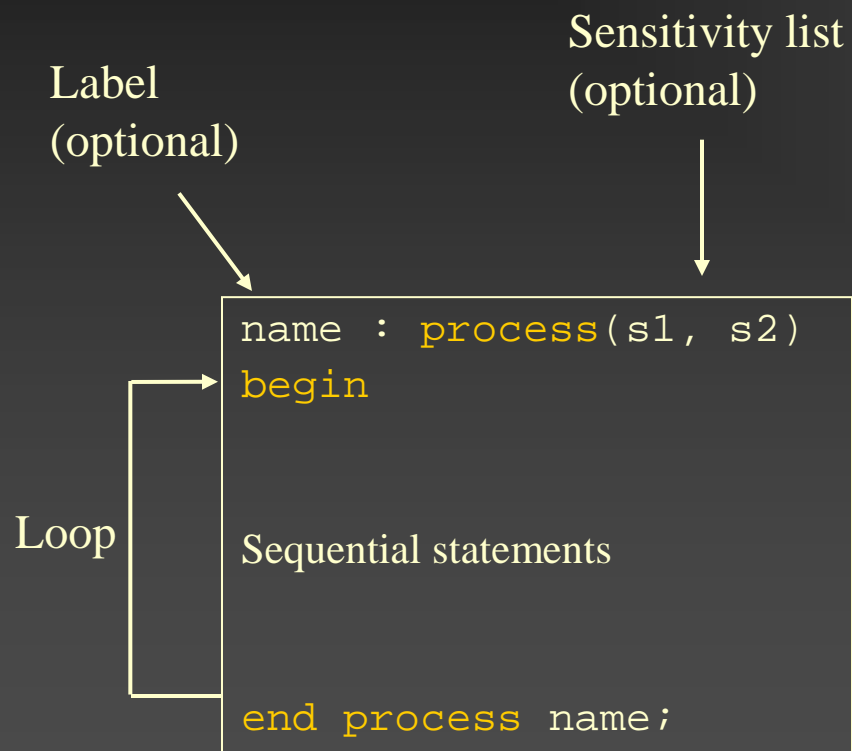

- Statements within a process are executed **sequentially**
- Execution „comparable“ to an **infinite loop**
- Execution controlled by the **sensitivity list** or **wait statements**
- A single architecture may have **multiple, concurrent processes**

Processes (2)



- ▶ Processes interchange information using signals.
- ▶ Assignments on signals are not done immediately, but at the next wait statement
⇒ Required for modeling parallel executions
- ▶ Signal assignments may trigger additional process executions

Wait Statements

- ▶ A single process may have **multiple wait statements (simulation)**
- ▶ or must have **exactly a single wait statement (synthesis)**

```
architecture beh of abc is
    signal s1, s2, s3 : bit;
begin
    p1: process
    begin
        s2 <= s1;
        s3 <= s2;
        wait on s1, s2;
    end process;
end architecture beh;
```

Simulation of Processes



- ▶ Execute all statements until a wait statement or the end of the process is reached
- ▶ If the end is reached, continue at the start of the process
- ▶ If a wait statement is reached suspend the execution of the process
 - If there is an active process
 - Resume that process
 - Otherwise
 - Increment simulation time

Sensitivity List



Special form of the **wait on** statement (at the **end** of the process)!

```
architecture beh of abc is
    signal s1, s2, s3 : bit;
begin
    p1: process (s1, s2)
        begin
            s2 <= s1;
            s3 <= s2;
            wait on s1, s2;
        end process;
    end architecture beh;
```

Sensitivity List



- ▶ Wait on at the end of a process is very common for synthesizable VHDL code!
- ▶ Therefore when writing synthesizable VHDL code, only sensitivity lists and no wait statements are normally used.
- ▶ For simulation of synthesizable VHDL code, the sensitivity list must **contain all signals** which are **read** by the process.
- ▶ Synthesis tools **ignore** the sensitivity list (only warning, if not complete).

Example Execution of a Process

```
architecture beh of abc is
  signal s1, s2, s3 : bit;
begin
  p1 : process(s1)
  begin
    s2 <= s1;
    s3 <= s2;
  end process;
end architecture beh;
```

Assumptions:

Before starting the simulation all signals have the value 0.

s1 changes from 0 to 1 → Process is started

s2 is marked to become 1 (s1's value)

s3 is marked to become 0 (s2's old value!)

Implicit wait on statement (sensitivity list)

The new values are assigned to s2 and s3

⇒ s2 becomes 1, s3 stays 0!

⇒ s2 and s3 have different values after the execution of the process!

WHY???

Example Execution of a Process

```
architecture beh of abc is
  signal s1, s2, s3 : bit;
begin
  p1 : process(s1, s2)
  begin
    s2 <= s1;
    s3 <= s2;
  end process;
end architecture beh;
```

Assumptions:

Before starting the simulation all signals have the value 0.

s1 changes from 0 to 1 → Process is started

s2 is marked to become 1 (s1's value)

s3 is marked to become 0 (s2's old value!)

Implicit wait on statement (sensitivity list)

The new values are assigned to s2 and s3

⇒ s2 becomes 1, s3 stays 0!

⇒ s2 and s3 have different values after the execution of the process!

Incomplete sensitivity list! s2 is missing

Architecture with 2 Processes

```
architecture beh of abc is
  signal s1, s2, s3, s4: bit;
begin
  and1 : process(s1, s2)
    if s1 = '1' and s2 = '1' then
      s3 <= '1';
    else
      s3 <= '0';
    end if;
  end process and1;
```


sequential

```
  and2 : process(s2, s3)
    if s2 = '1' and s3 = '1' then
      s4 <= '1';
    else
      s4 <= '0';
    end if;
  end process and2;
```

sequential

```
end architecture beh;
```

Parallel

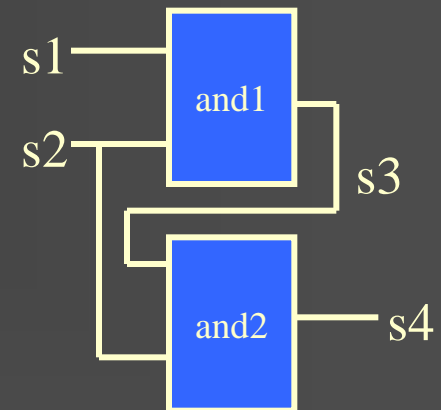

Manual Simulation

```
architecture beh of abc is
  signal s1, s2, s3, s4: bit;
begin
  and1 : process(s1, s2)
    if s1 = `1` and s2 = `1` then
      s3 <= `1`;
    else
      s3 <= `0` ;
    end if;
  end process and1;

  and2 : process(s2, s3)
    if s2 = `1` and s3 = `1` then
      s4 <= `1`;
    else
      s4 <= `0`;
    end if;
  end process and2;
end architecture beh;
```

Assumptions:

$s1 = 0$

$s2 = 1$

$\Rightarrow s3 = 0$

$\Rightarrow s4 = 0$

Manual Simulation

```
architecture beh of abc is
  signal s1, s2, s3, s4: bit;
begin
  and1 : process(s1, s2)
    if s1 = '1' and s2 = '1' then
      s3 <= '1';
    else
      s3 <= '0';
    end if;
  end process and1;

  and2 : process(s2, s3)
    if s2 = '1' and s3 = '1' then
      s4 <= '1';
    else
      s4 <= '0';
    end if;
  end process and2;
end architecture beh;
```

Assumptions:

$s1 = 0$

$s2 = 1$

$\Rightarrow s3 = 0$

$\Rightarrow s4 = 0$

$s1: 0 \rightarrow 1$

Manual Simulation

```
architecture beh of abc is
  signal s1, s2, s3, s4: bit;
begin
  and1 : process(s1, s2)
    if s1 = '1' and s2 = '1' then
      s3 <= '1';
    else
      s3 <= '0' ;
    end if;
  end process and1;

  and2 : process(s2, s3)
    if s2 = '1' and s3 = '1' then
      s4 <= '1';
    else
      s4 <= '0';
    end if;
  end process and2;
end architecture beh;
```

Assumptions:

$s1 = 0$

$s2 = 1$

$\Rightarrow s3 = 0$

$\Rightarrow s4 = 0$

$s1: 0 \rightarrow 1$

$\Rightarrow s3: 0 \rightarrow 1$

Manual Simulation

```
architecture beh of abc is
  signal s1, s2, s3, s4: bit;
begin
  and1 : process(s1, s2)
    if s1 = '1' and s2 = '1' then
      s3 <= '1';
    else
      s3 <= '0' ;
    end if;
  end process and1;

  and2 : process(s2, s3)
    if s2 = '1' and s3 = '1' then
      s4 <= '1';
    else
      s4 <= '0';
    end if;
  end process and2;
end architecture beh;
```

Assumptions:

$s1 = 0$

$s2 = 1$

$\Rightarrow s3 = 0$

$\Rightarrow s4 = 0$

$s1: 0 \rightarrow 1$

$\Rightarrow s3: 0 \rightarrow 1$

$\Rightarrow s4: 0 \rightarrow 1$

Another Example

```
entity abc is
  port
  (
    A, B, C : in  bit;
    Z, R    : out bit
  );
end entity abc;

architecture beh of abc is
  signal X, Y : bit;
begin
  process(A, B, C)
  begin
    X <= A;
    Y <= B;
    Z <= X and Y;
    Y <= C;
    R <= X and Y;
  end process;
end architecture beh;
```

Which values are assigned to Z and R?

Another Example

```
entity abc is
  port
  (
    A, B, C : in bit;
    Z, R    : out bit
  );
end entity abc;

architecture beh of abc is
  signal X, Y : bit;
begin
  process(A, B, C)
  begin
    X <= A;
    Y <= B;
    Z <= X and Y;
    Y <= C;
    R <= X and Y;
  end process;
end architecture beh;
```

Which values are assigned to Z and R?

After a single process execution
Z and R are set to X_{old} and Y_{old}.

After **completing the sensitivity list** (adding X and Y), a second execution of the process is triggered.

R and Z are set to A and C after the second iteration.

Attention:
Z is NEVER set to A and B

Simple Signal Assignment Example

- ▶ Simple signal assignment is much too complicated:

```
assign : process(s1, s2)
    s3 <= s1 and s2;
end process assign;
```

- ▶ Is there an easier way?
- ▶ Yes:
 - ▶ Short form for signal assignment (named concurrent signal assignment):

```
s3 <= s1 and s2;
```

Concurrent Signal Assignments



- ▶ **Outside** of a process
- ▶ Possibility for specifying a **delay**
- ▶ Possibility for **conditional** assignments
- ▶ Possibility for **selective** assignments
- ▶ **Parallel execution** (short form of a process declaration)


Concurrent Signal Assignments

Unconditional assignment

Conditional Assignment

Selective Assignment
 
```
architecture beh of abc is
  signal s1, s2, s3, s4, s5: bit;
begin
  and1 : s3 <= s1 and s2;
  and2 : s4 <= '1' when s3='1' and s2 ='1'
        else '0';
  inverter : with s4 select
              output <= '1' when '0',
                    '0' when '1';
end architecture beh;
```



Signal Delay

- ▶ Delays are modeled as follows:

```
s3 <= s1 and s2 after 1 ns;
```

⇒ Applicable only in **Behavioral Simulation!**

- ▶ Not **synthesizable**, ignored by the synthesis tool.
- ▶ After **technology mapping**, real hardware **delays** added to simulation netlist.

Behavioral Modeling - Summary



- ▶ Based on **processes**
- ▶ **Multiple** processes per architecture
- ▶ Multiple processes executed **concurrently**
- ▶ Processes executed **sequentially**
- ▶ Controlled by **wait** statements (**simulation**)
- ▶ **Simplifications:**
 - Sensitivity list instead of wait on
 - Concurrent signal assignments

Contents




- ▶ Structural Modeling
 - Instantiation of Components
- ▶ Behavioral Modeling
 - Processes
 - Concurrent Signal Assignments
- ▶ Mixed Modeling

Mixed Modeling (1)

- ▶ Behavioral- and structural Descriptions may be mixed in the same architecture
- ▶ Descriptions on different layers of abstraction may be mixed

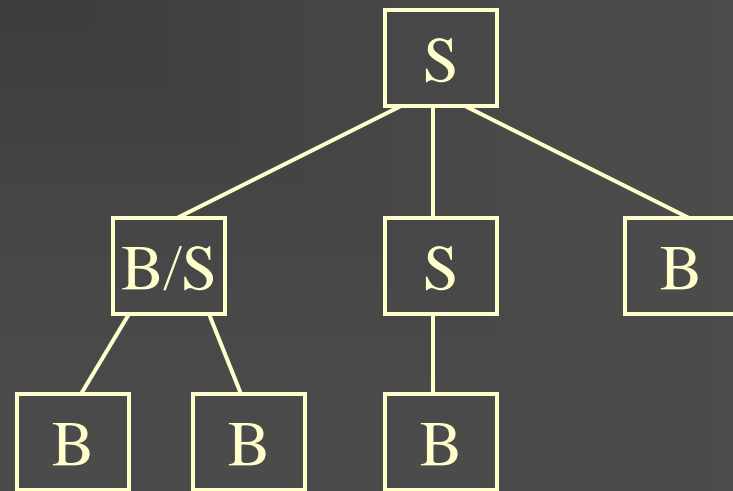S ... Structural Description
B ... Behavioral Description
S/B ... Mixed Behavioral/
Structural Description




Mixed Modeling (1)

- ▶ Behavioral- and structural Descriptions may be mixed in the same architecture
- ▶ Descriptions on different layers of abstraction may be mixed

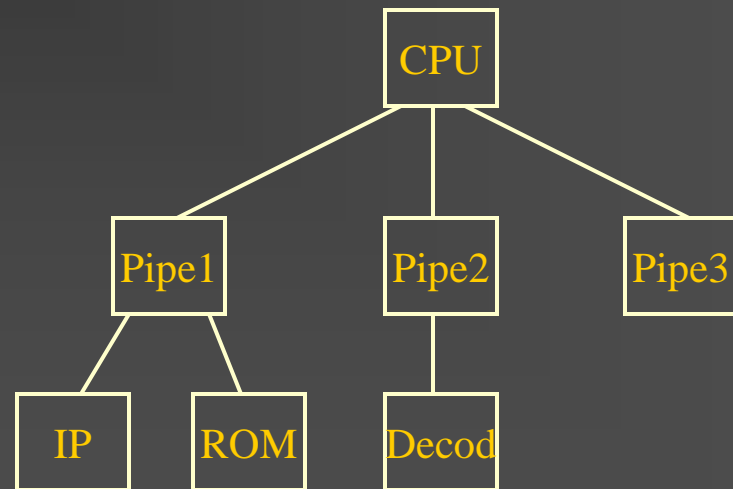
Example of a CPU

Break down into subsystems
⇒ Integration of subsystems as components



Mixed Modell (2)

	<pre>architecture beh of abc is signal s1, s2, s3, s4, s5 : bit; begin</pre>
Structural	<pre> and1 : one generic map(DEPTH => 10) port map(a => s1, b => s2, c => s3);</pre>
Behavioral RTL level	<pre> process(s3) begin if s3='1' then s4 <= '0'; else s4 <= '1'; end if; end process;</pre>
Behavioral Logic level	<pre> s5 <= s1 xor s4;</pre>
	<pre>end architecture beh;</pre>

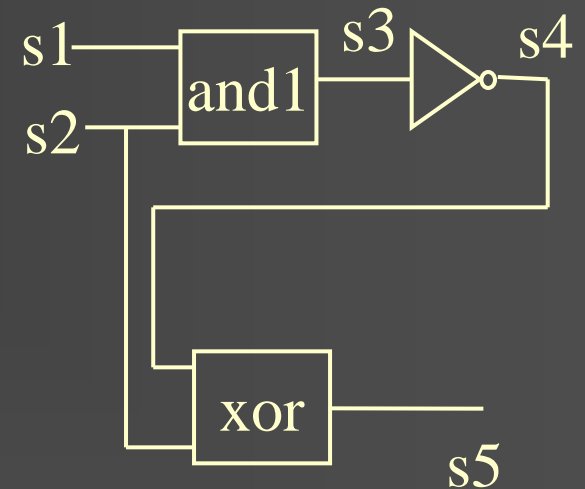



Summary

```
architecture xyz of abc is  
begin
```

Behavioral

```
if A = '1' then    D <= NOT E  
    B <= B+1  
else  
    B <= B  
end if  
                  F <= D OR B  
                  C <= F AND A
```

Structural

  

```
end architecture xyz;
```

Summary



```
architecture xyz of abc is  
begin
```

Behavioral

Processes

- Processes are running in parallel
- Statements of a process are executed sequentially
- Controlled by wait statements

Simplifications

- Concurrent signal assignments
 - Unconditional, conditional, selective
 - Outside of Processes
- Sensitivity lists

Structural

Components

- Declaration
 - Package or architecture
- Instantiation
 - Port mapping, generic mapping
- Configuration
 - Configuration file

```
end architecture xyz ;
```

