

Hardware Modeling



Advanced Synthesis

*Vienna University of Technology
Department of Computer Engineering
ECS Group*

Contents

- Memory instances
- Common synthesis pitfalls
- Live Demo

Memory Instances

► ROM

- Asynchronous
- Synchronous

► RAM

- Single Port (rw)
- Dual Port (r/rw)
- Triple Port (r/r/w)

Asynchronous ROM



```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity async_rom is
  port
  (
    address : in std_logic_vector(7 downto 0);
    data     : out std_logic_vector(7 downto 0)
  );
end entity async_rom;
```

Asynchronous ROM

```
architecture beh of async_rom is
    subtype ROM_ENTRY_TYPE is std_logic_vector(7 downto 0);
    type ROM_TYPE is array (0 to (2 ** 8) - 1) of ROM_ENTRY_TYPE;
    constant rom : ROM_TYPE :=
    (
        0 => x"FF", 1 => x"AA", 30 => x"55", ...,
        others => x"00"
    );
begin
    process(address)
    begin
        data <= rom(to_integer(unsigned(address)));
    end process;
end architecture beh;
```

Synchronous ROM



```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity sync_rom is
  port
  (
    clk      : in std_logic;
    address : in std_logic_vector(7 downto 0);
    data     : out std_logic_vector(7 downto 0)
  );
end entity sync_rom;
```

Synchronous ROM

```
architecture beh of sync_rom is
  subtype ROM_ENTRY_TYPE is std_logic_vector(7 downto 0);
  type ROM_TYPE is array (0 to (2 ** 8) - 1) of ROM_ENTRY_TYPE;
  constant rom : ROM_TYPE :=
  (
    0 => x"FF", 1 => x"AA", 30 => x"55", ...,
    others => x"00"
  );
begin
  process(clk)
  begin
    if rising_edge(clk) then
      data <= rom(to_integer(unsigned(address)));
    end if;
  end process;
end architecture beh;
```

Synchronous Single Port RAM

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity sp_ram is
    generic
    (
        ADDR_WIDTH : integer range 1 to integer'high;
        DATA_WIDTH : integer range 1 to integer'high
    );
    port
    (
        clk      : in  std_logic;
        address  : in  std_logic_vector(ADDR_WIDTH - 1 downto 0);
        data_out : out std_logic_vector(DATA_WIDTH - 1 downto 0);
        wr       : in  std_logic;
        data_in  : in  std_logic_vector(DATA_WIDTH - 1 downto 0)
    );
end entity sp_ram;
```

Synchronous Single Port RAM

```
architecture beh of sp_ram is
    subtype RAM_ENTRY_TYPE is std_logic_vector(DATA_WIDTH - 1 downto 0);
    type RAM_TYPE is array (0 to (2 ** ADDR_WIDTH) - 1) of RAM_ENTRY_TYPE;
    signal ram : RAM_TYPE := (others => x"00");
begin
    process(clk)
    begin
        if rising_edge(clk) then
            data_out <= ram(to_integer(unsigned(address)));
            if wr = '1' then
                ram(to_integer(unsigned(address))) <= data_in;
            end if;
        end if;
    end process;
end architecture beh;
```

Synchronous Dual Port RAM

```
library ieee; use ieee.std_logic_1164.all; use ieee.numeric_std.all;

entity dp_ram is
generic
(
    ADDR_WIDTH : integer range 1 to integer'high;
    DATA_WIDTH : integer range 1 to integer'high
);
port
(
    clk      : in  std_logic;
    address1 : in  std_logic_vector(ADDR_WIDTH - 1 downto 0 );
    data_out1 : out std_logic_vector(DATA_WIDTH - 1 downto 0 );
    wr1      : in  std_logic;
    data_in1 : in  std_logic_vector(DATA_WIDTH - 1 downto 0 );
    address2 : in  std_logic_vector(ADDR_WIDTH - 1 downto 0 );
    data_out2 : out std_logic_vector(DATA_WIDTH - 1 downto 0 )
);
end entity dp_ram;
```

Synchronous Dual Port RAM

```
architecture beh of dp_ram is
    subtype RAM_ENTRY_TYPE is std_logic_vector(DATA_WIDTH - 1 downto 0);
    type RAM_TYPE is array (0 to (2 ** ADDR_WIDTH) - 1) of RAM_ENTRY_TYPE;
    signal ram : RAM_TYPE := (others => x"00");
begin
    process(clk)
    begin
        if rising_edge(clk) then
            data_out1 <= ram(to_integer(unsigned(address1)));
            data_out2 <= ram(to_integer(unsigned(address2)));
            if wr1 = '1' then
                ram(to_integer(unsigned(address1))) <= data_in1;
            end if;
        end if;
    end process;
end architecture beh;
```

Synchronous Triple Port RAM

```
library ieee; use ieee.std_logic_1164.all; use ieee.numeric_std.all;

entity tp_ram is
generic
(
    ADDR_WIDTH : integer range 1 to integer'high;
    DATA_WIDTH : integer range 1 to integer'high
);
port
(
    clk                     : in std_logic;
    address1, address2, address3 :
        in std_logic_vector(ADDR_WIDTH - 1 downto 0);
    data_in1                 :
        in std_logic_vector(DATA_WIDTH - 1 downto 0);
    wr1                     : in std_logic;
    data_out2, data_out3     :
        out std_logic_vector(DATA_WIDTH - 1 downto 0)
);
end entity tp_ram;
```

Synchronous Triple Port RAM

```
architecture beh of tp_ram is
    subtype RAM_ENTRY_TYPE is std_logic_vector(DATA_WIDTH - 1 downto 0);
    type RAM_TYPE is array (0 to (2 ** ADDR_WIDTH) - 1) of RAM_ENTRY_TYPE;
    signal ram : RAM_TYPE := (others => x"00");
begin
    process(clk)
    begin
        if rising_edge(clk) then
            data_out2 <= ram(to_integer(unsigned(address2)));
            data_out3 <= ram(to_integer(unsigned(address3)));
            if wr1 = '1' then
                ram(to_integer(unsigned(address1))) <= data_in1;
            end if;
        end if;
    end process;
end architecture beh;
```

Contents

- ▶ Memory instances
- ▶ Common synthesis pitfalls
- ▶ Live Demo



Common Synthesis Pitfalls

- ▶ Complexity
- ▶ Latches



Complexity

- and
- add
- mul
- div
- mod

Complexity

```
entity operation is
  port
  (
    a, b: in std_logic_vector(31 downto 0);
    o   : out std_logic_vector(31 downto 0)
  );
end entity operation;
```

```
architecture beh of operation is
begin
  o <= a OPERATION b;
end architecture beh;
```


Complexity - AND

► $o \leq a \text{ and } b;$




Complexity - ADD

► $0 \leq a + b;$

 


Complexity - MUL

► $0 \leq a * b;$

 


Complexity - DIV

► $0 \leq a / b;$

 

Complexity - MOD

► $0 \leq a \bmod b;$

 

Complexity - Results

Operation	Estim. Frequency	# LUTs	#DSP Blocks à 8 9-bit multiplier
and	845 MHz	32	0
add	320 MHz	32	0
mul	250 MHz	0	1
div	14 MHz	2152	0
mod	7 MHz	2220	0

Latches

```
process(i1, i2, i3)
begin

    if i1 = '1' and i2 = '1' then
        o <= i3;
    end if;
end process;
```

Latches

```
process(i1, i2, i3)
begin


    if i1 = '1' and i2 = '1' then
        o <= i3;
    end if;
end process;
```

```
+ [i] Info: Only one processor detected - disabling parallel compilation
+ [i] Info: Found 2 design units, including 1 entities, in source file latch.vhd
+ [i] Info: Elaborating entity "latch1" for the top level hierarchy
+ [!] Warning (10631): VHDL Process Statement warning at latch.vhd(14): inferring latch(es) for signal or variable "o", which holds
+ [i] Info (10041): inferred latch for "o" at latch.vhd(14)
+ [i] Info: Implemented 6 device resources after synthesis - the final resource count might be different
```

Latches


```
process(i1, i2, i3)
begin

     if i1 = '1' and i2 = '1' then
        o <= i3;
    end if;
end process;
```



Latches

 
```
process(i1, i2, i3)
begin
    o <= '0';
    if i1 = '1' and i2 = '1' then
        o <= i3;
    end if;
end process;
```




Contents

- ▶ Memory instances
- ▶ Common synthesis pitfalls
- ▶ Live Demo

Live Demo - Debouncing

 

Live Demo - Debouncing

 




Live Demo - Debouncing

Inputs: i/cnt

Outputs: o/clear_cnt

 

Live Demo - Debouncing

Inputs: i/cnt

Outputs: o/clear_cnt


State	Output	Condition	Next state
idle0	0/1	1/X	timeout0
timeout0	0/0	0/X	idle0
		1/CNT_MAX	idle1
idle1	1/1	0/X	timeout1
timeout1	1/0	1/X	idle1
		0/CNT_MAX	idle0

Live Demo - Debouncing




► Design Entry

Live Demo - Debouncing

 

Live Demo - Debouncing

 

► Synthesis: Quartus

Additional Literature

► Device specific guidelines

- Device datasheets
- Manufacturer user guides and recommendations

► Platform specific guidelines

- Board datasheet

► VHDL language guide

- Peter Ashenden - The Designer's Guide to VHDL, 3rd edition

Summary

- Memory instances
- Common synthesis pitfalls
 - Complexity
 - Latches
- Live Demo